

# Capacitive Mains Inputs; choosing capacitor and resistor combinations for 120 V a.c. 240 V a.c and 50 and 60Hz

R.P. clark

June 27, 2018

## Abstract

Calculations to work out capacitance values to drive an opto-coupler to detect mains voltage for 50 to 60 Hz.

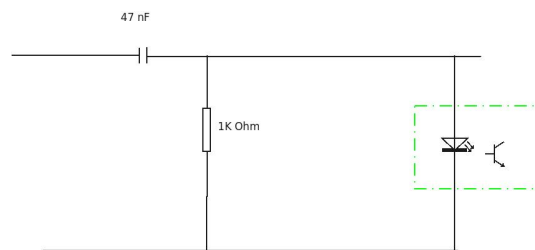


Figure 1: Opto-coupled mains input circuit

## 1 Opto coupler circuit

This circuit is used to detect mains voltage via a capacitor and a resistor forming a potential divider so that a lower voltage can be used to drive an opto-isolator that protects the processor reading the signal.

## 2 Calculations

A potential divider using a capacitor and a resistor is used to lower mains voltage to levels that can drive a typical opto-coupler input ( $\approx 2V$ ).

A potential divider using a capacitor and resistor means using the complex identity for the capacitors reactance,  $X$ .

$$X = \frac{-j}{\omega C}$$

The  $\omega C$  term is dependent on frequency and is equivalent to  $2.\pi.f$  .

Using a potential divider to determine the voltage over the resistor gives:

$$V_{out} = V_{in} \times \frac{R}{R - \frac{j}{2\pi \cdot f \cdot C}}$$

The equation above leaves a complex divisor. To get a complex number as the numerator, the denominator and numerator must be multiplied by the conjugate of the denominator, thus:

$$\frac{R}{R - \frac{j}{2\pi \cdot f \cdot C}} \equiv \frac{R \times \left(R + \frac{j}{2\pi \cdot f \cdot C}\right)}{\left(R - \frac{j}{2\pi \cdot f \cdot C}\right) \times \left(R + \frac{j}{2\pi \cdot f \cdot C}\right)}$$

This leaves a real number as the denominator, i.e.  $R^2 + \frac{1}{2\pi \cdot f \cdot C}^2$ . The resulting complex number,  $X$ ,

$$X = \frac{R \times \left(R + \frac{j}{2\pi \cdot f \cdot C}\right)}{R^2 + \frac{1}{2\pi \cdot f \cdot C}^2}$$

or,

$$X = \frac{R^2 + \left(R \frac{j}{2\pi \cdot f \cdot C}\right)}{R^2 + \frac{1}{2\pi \cdot f \cdot C}^2} \quad (1)$$

can now be evaluated for phase and magnitude. Equation 1 can be generally applied to potential dividers in figure 1.

## 2.1 Example calculation

At 50Hz with 240 V a.c. applied, with R at 1000 Ohms and C at 47 nF

$$\begin{aligned} & \frac{1000^2 + \left(1000 \frac{j}{2\pi \cdot 50 \cdot 47e-9}\right)}{R^2 + \frac{1}{2\pi \cdot 50 \cdot 47e-9}^2} \\ & \frac{1000^2 + \left(1000 \times 67726j\right)}{1000^2 + 67726^2} \\ & \frac{1000^2 + \left(67726000j\right)}{4.5877 \times 10^9} \end{aligned}$$

This gives a complex number

$$\frac{1000^2 + 67726000j}{4.5877 \times 10^9}$$

i.e.

$$(216 \times 10^{-6} + 14.76 \times 10^{-3}j) .$$

This complex number has a magnitude of 0.0147 and an argument of 89.15 degrees (which is expected as most of the reactance comes from the capacitor). So with 240 V a.c. applied (RMS) the opto would see a signal with  $0.0147 \times 240 = 3.54V(RMS)$

### 3 plotting the voltage at the opto-coupler

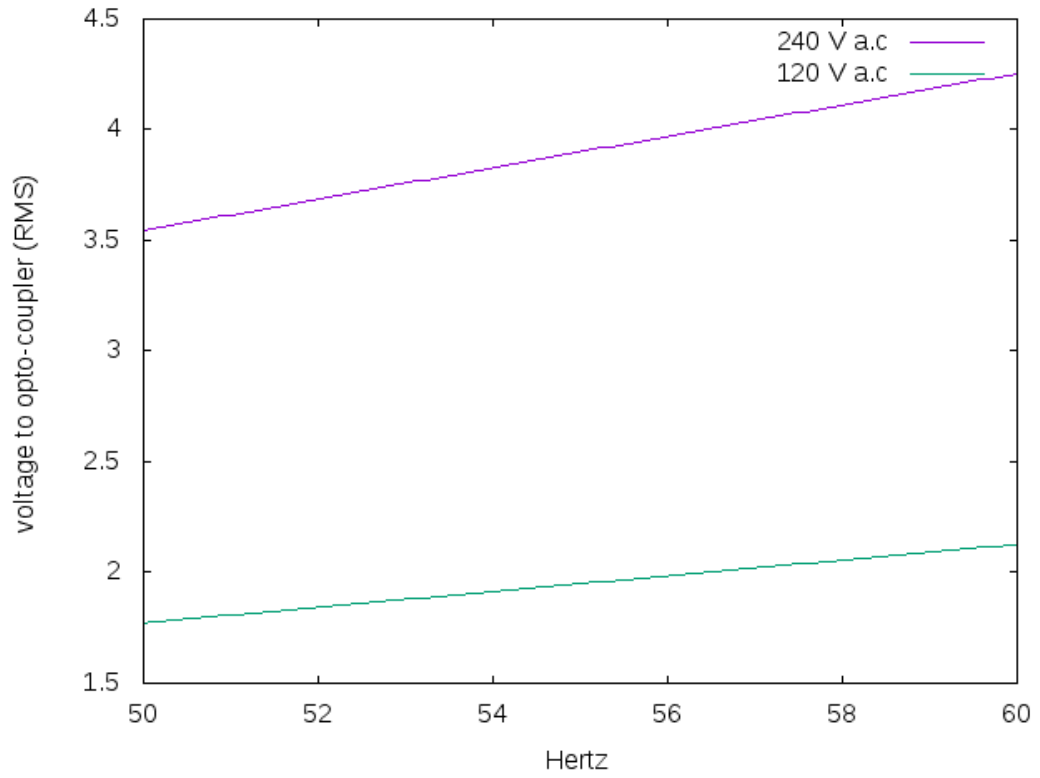


Figure 2: RMS voltage seen at opto-coupler for 50 to 60 Hz range

### 3.1 plotting the voltage at the opto-coupler: gnuplot scripts

```
#####  
#  
p=3.14159265358979323844  
#  
# 47nF  
C=47e-9  
#  
# 1k Ohms  
R=1000  
  
# define complex operator  
j={0,1}  
  
set xlabel "Hertz"  
set ylabel "Resistance"  
  
# x is the frequency  
set xrange[50:60]  
  
# z(x) is the reactance  
z(x)=(j/(2*p*x*C))  
  
# denominator  
d(x)=(R*R+z(x)*z(x))  
  
# numerator  
n(x)=(R*R+R*z(x))  
  
plot abs(z(x)) title "reactance over capacitor"  
!sleep 4  
  
set ylabel "denominator value (abs)"  
plot abs(d(x))  
!sleep 4  
  
set ylabel "numerator value (abs)"  
plot abs(n(x))  
!sleep 4  
  
v(x)=abs((n(x))/(d(x)))  
  
# gives large numbers h(x)=arg((n(x))/(d(x)))  
  
set ylabel "voltage to opto-coupler (RMS)"  
plot 240*v(x) title "240 V a.c", 120*v(x) title "120 V a.c"  
!sleep 4  
  
set terminal png  
set output "RMS_volts_to_opto.png"  
plot 240*v(x) title "240 V a.c", 120*v(x) title "120 V a.c"  
  
#set angles degrees  
#set label "phase change in mains over opto"  
#plot 240*h(x) title "240 V a.c", 120*h(x) title "120 V a.c"  
#!sleep 4  
#
```

typeset in L<sup>A</sup>T<sub>E</sub>X June 27, 2018.